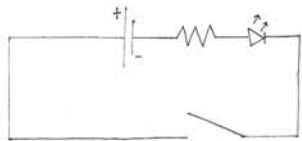


$$R = \frac{V}{I}$$
$$R = \frac{(4.5 - 2)}{0.02} = 125 \Omega$$

Nota: $V_{LED} = 2V$, $I_{LED} = 0.02A$



[Model alàmbic amb il·luminació]