


**ETSETB. RADIATION AND PROPAGATION. Test: basic concepts on linear circuits**

Name:	ID						
	Code	X	Y		Z		

Each datum values one point: 8 points total.

TEST CODE: X=      Y=      Z=

P1.- The circuit at the right works in sinusoidal steady state. The source open circuit voltage is given by  $V_g = 10e^{j\frac{\pi}{2}}$  V. The voltage and current phasors at the load are  $V_L = |V_L|e^{j\varphi_V}$  and  $I_L = |I_L|e^{j\varphi_I}$  respectively. **All values are rms.** Find the following magnitudes:

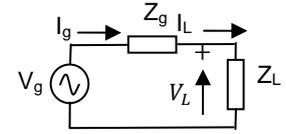

Z=1 or 2:	Z= 3 or 4	Z= 5 or 6	Z= 7 or 8	Z=9 or 0
$Z_L=(20+X)\cdot(1+j) \Omega$	$Z_g=(30+X)\cdot(1-j) \Omega$	$Z_L=(40-X)\cdot(1+j) \Omega$	$Z_g=(40-X)\cdot(1+j) \Omega$	$Z_L=(30-X)\cdot(1-j) \Omega$
$V_L=-10\cdot(1-j) V_e$	$I_L=90\cdot(1+j) mA_e$	$Z_g=(20+X)\cdot(1-j) \Omega$	$V_L=5-3j V_e$	$Z_g=(20+X)\cdot(1+j) \Omega$
$I_L=$ _____ mA <sub>e</sub>	$V_L=$ _____ V <sub>e</sub>	$V_L=$ _____ V <sub>e</sub>	$I_L=$ _____ mA <sub>e</sub>	$I_L=$ _____ mA <sub>e</sub>
$Z_g=$ _____ $\Omega$	$Z_L=$ _____ $\Omega$	$ I_L =$ _____ mA <sub>e</sub>	$Z_L=$ _____ $\Omega$	$ V_L =$ _____ V <sub>e</sub>
		$\varphi_I$ _____ deg		$\varphi_V$ _____ deg


(\*Each section values 2 points regardless of the number of requested values

P2.- In a circuit similar to the one given in the previous exercise, find the power delivered to the load,  $P_L$  (mW), taking into account the following parameters:

Z=1 or 2:	Z= 3 or 4	Z= 5 or 6	Z= 7 or 8	Z=9 or 0
$Z_L=(30+Y)\cdot(1+j) \Omega$	$Y_L=(40+Y)\cdot(2-j) mS^{(*)}$	$V_L=(30-Y)\cdot(2+j) V_e$	$Y_L=(30+Y)\cdot(1+j) mS^{(*)}$	$Z_L=(40-Y)\cdot(2+j) \Omega$
$V_L=20\cdot(1+2j) V_e$	$I_L=700\cdot(1+2j) mA_e$	$I_L=4Y0\cdot(3-j) mA_e$	$I_L=400\cdot(2+j) mA_e$	$V_L=30\cdot(2-j) V_e$
$P_L=$ _____ W	$P_L=$ _____ W	$P_L=$ _____ W	$P_L=$ _____ W	$P_L=$ _____ W



(\*mS=miliSiemens. Voltage and current values are RMS

P3.- A generator works at a frequency  $f=5X0$  MHz in a sinusoidal steady state. Its internal impedance is  $R_g=50 \Omega$  and its rms open circuit voltage is  $V_g=(10+Y) V$ . The source is loaded with a reactive impedance  $Z_L$  ( $Z_L=1/Y_L$ ) given by one of the configuration RC or RL detailed in the right figure ( $R=100 \Omega$ ,  $L = \frac{100}{\pi}$  nH and  $C = \frac{20}{\pi}$  pF). Find the value of this complex load ( $Z_L$  o  $Y_L$ ) and the power  $P_L$  (mW) that the source is delivering to it.

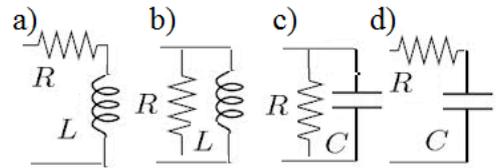

Z=1 or 2:	Z= 3 or 4	Z= 5 or 6	Z= 7 or 8	Z=9 or 0
<b>Case a)</b>	<b>Case b)</b>	<b>Case c)</b>	<b>Case d)</b>	<b>Case a)</b>
$Y_L=$ _____ mS <sup>(*)</sup>	$Z_L=$ _____ $\Omega$	$Z_L=$ _____ $\Omega$	$Y_L=$ _____ mS <sup>(*)</sup>	$Y_L=$ _____ mS <sup>(*)</sup>
$P_L=$ _____ mW	$P_L=$ _____ mW	$P_L=$ _____ mW	$P_L=$ _____ mW	$P_L=$ _____ mW

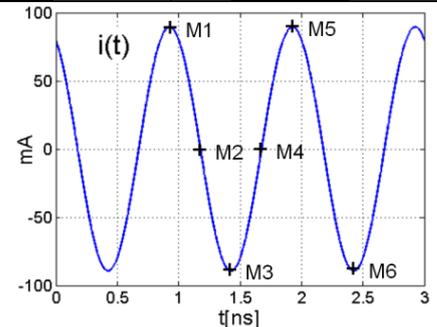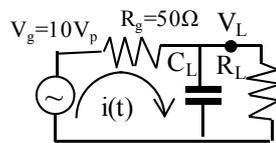P4.- The RC load in the figure at the right is fed by means of a generator with open circuit voltage given by  $V_g(t) = 10 \cdot \cos(\omega t)$  V and internal impedance  $R_g=50 \Omega$ . The current  $i(t) = I_p \cos(\omega t + \varphi_I)$  mA supplied by the generator is measured with an oscilloscope that gives the screen markers M1 to M6. If  $V_L(t) = V_p \cos(\omega t + \varphi_V)$  find:



Z=1 or 2:	Z= 3 or 4	Z= 5 or 6	Z= 7 or 8	Z=9 or 0
M1=[0,9254, 89,44]	M4=[1,676, 0]	M2=[1,176, 0]	M3=[1,426, -89,44]	M5=[1,926, 89,44]
M3=[1,426, -89,44]	M5=[1,926, 89,44]	M3=[1,426, -89,44]	M6=[2.426, -89,44]	M6=[2.426, -89,44]
$f=$ _____ MHz	$f=$ _____ MHz	$f=$ _____ MHz	$f=$ _____ MHz	$f=$ _____ MHz
$\varphi_I =$ _____ deg	$I_p =$ _____ (mA rms)	$\varphi_I =$ _____ rad	$\varphi_I =$ _____ deg	$I_p =$ _____ (mA peak)
$\varphi_I \in [0, 360^\circ]$	$\varphi_V =$ _____ rad	$\varphi_I \in [0, 2\pi]$ rad	$\varphi_I \in [0, 360^\circ]$	$\varphi_V =$ _____ deg
$V_p=$ _____ V (peak)	$\varphi_V \in [0, 2\pi]$ rad	$V_p=$ _____ V (rms)	$V_p=$ _____ V (peak)	$\varphi_V \in [0, 360^\circ]$

Optional: Find the value of  $C_L$  (pF) and  $R_L$  ( $\Omega$ )

SOLUTIONS CORRECTION FOR SEVERAL CODES X-Y-Z

CODIGO PRUEBA: X=1 Y=2 Z=3

PROBLEMA 1

DATOS  $V_g=0+10i$  Ve,  $Z_g=31-31i$  Ohm.  $I_L=90+90i$  mAe

SOL P1  $V_L=-5.6+10i$  Ve.  $Z_L=24.6+86.6i$  Ohm

PROBLEMA 2

DATOS P2:  $Y_L=84-42i$  mS,  $I_L=700+1400i$  mAe

SOL P2  $P_L=23.3$  W

PROBLEMA 3

DATOS P3:  $f=510$  MHz,  $V_g=12$  Ve

SOL P2  $Z_L=51+50i$  Ohm,  $P_L=578.2$  mW

PROBLEMA 4

SOL P3  $f=1000$  MHz,  $I_p=63.2$  mA eficaces,  $\phi_V=5.96$  rad

SOL Opcional  $R_L=100.3$  Ohm,  $C_L=5/\pi$  pF

%%%

CODIGO PRUEBA: X=3 Y=4 Z=5

PROBLEMA 1

DATOS  $V_g=0+10i$  Ve,  $Z_L=37+37i$  Ohm.  $Z_g=23-23i$  Ohm

SOL P1  $V_L=-4.5+7.2i$  Ve.  $I_{Lmod}=162.3$  mAe, Fase  $I_L=76.9$  grados

PROBLEMA 2

DATOS P2:  $V_L=52+26i$  Ve,  $I_L=1320-440i$  mAe

SOL P2  $P_L=57.2$  W

PROBLEMA 3

DATOS P3:  $f=530$  MHz,  $V_g=14$  Ve

SOL P2  $Z_L=18.2-38.6i$  Ohm,  $P_L=581$  mW

PROBLEMA 4

SOL P3  $f=1000$  MHz,  $\phi_I=0.46$ rad,  $V_p=4.5$  V eficaces

SOL Opcional  $R_L=100.3$  Ohm,  $C_L=5/\pi$  pF

%%%

CODIGO PRUEBA: X=5 Y=6 Z=7

PROBLEMA 1

DATOS  $V_g=0+10i$  ve,  $Z_g=35+35i$  Ohm.  $V_L=5-3i$  Ve

SOL P1  $I_L=114.3+257.1i$  mAe.  $Z_L=-2.5-20.6i$  Ohm

PROBLEMA 2

DATOS P2:  $Y_L=36+36i$  mS,  $I_L=400+200i$  mAe

SOL P2  $P_L=2.8$  W

PROBLEMA 3

DATOS P3:  $f=550$  MHz,  $V_g=16$  Ve

SOL P2  $Y_L=8.3+3.8i$  mS,  $P_L=1042.1$  mW

PROBLEMA 4

SOL P3  $f=1000$  MHz,  $\phi_I=26.6^\circ$ ,  $V_p=6.3$  V pico

SOL Opcional  $R_L=100.3$  Ohm,  $C_L=5/\pi$  pF

## CODIGO MATLAB PARA LA CORRECCION DEL PROBLEMA SEGUN VARIABLES X-Y-Z

```
%Problemas_Circuitos_Lineales.m
% Código para generar los datos y las soluciones del tema introductorio de Circuitos Lineales
%Francesc Torres 01/02/2014
clear
flag_loop_ON=1; %1 siempre para mantenerse en el bucle de correccion. Salida bucle con CTRL-C
flag_control=input('Entrar 1 para visualizar el cálculo de control, 0 para omitirlo. Control=');

%Inicio bucle correccion con entrada codigo

while flag_loop_ON==1

%CODIGO PRUEBA
disp(' ')
disp(' ')
disp('CORRECCIÓN PROBLEMA CIRCUITOS LINEALES (press CTRL-C to end)');
XYZ=input('CODIGO PRUEBA (3 cifras)= ');
X=floor(XYZ/100);
Y=floor((XYZ-100*X)/10);
Z=XYZ-100*X-10*Y;
disp(['CODIGO PRUEBA: X=', num2str(X), ' Y=', num2str(Y), ' Z=', num2str(Z)])
disp(' ')
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
disp(' ')
switch_cases=Z;

%DATOS COMUNES PROBLEMAS
disp('PROBLEMA 1')
%PROBLEMA 1
Vg=10*exp(1i*pi/2); %Tensión generador en c.a.

switch switch_cases
    case {1,2}
        ZL=(20+X)*(1+1i);
        VL=-10*(1-1i);
        Zg=(Vg/VL-1)*ZL;
        IL=VL/ZL;
        disp(['DATOS Vg=', num2str(round(10*Vg)/10), ' Ve, ZL=', num2str(ZL), ' Ohm. VL=',
num2str(VL), ' Ve']);
        disp(['SOL P1 IL=', num2str(round(10*IL*1e3)/10), ' mAe. Zg=', num2str(round(10*Zg)/10),
Ohm]);
        %control
        if flag_control==1
            ZLctl=Zg*VL/(Vg-VL);
            VLctl=Vg-IL*Zg;
            Vgctl=VL+IL*Zg;
            disp(['CTL P1 Vg=', num2str(round(10*Vgctl)/10), ' Ve, ZL=', num2str(ZLctl), ' Ohm, VL=',
num2str(VLctl), ' Ve']);
        end
    case {3,4}
        Zg=(30+X)*(1-1i);
        IL=90*(1+1i)*1e-3;
        VL=Vg-IL*Zg;
        ZL=VL/IL;
        disp(['DATOS Vg=', num2str(round(10*Vg)/10), ' Ve, Zg=', num2str(Zg), ' Ohm. IL=',
num2str(IL*1e3), ' mAe']);
        disp(['SOL P1 VL=', num2str(round(10*VL)/10), ' Ve. ZL=', num2str(round(10*ZL)/10), ' Ohm']);
        %control
        if flag_control==1
            Zgctl=ZL*(Vg-VL)/VL;
            Vgctl1=VL+IL*Zgctl; Vgctl2=VL*(ZL+Zgctl)/ZL;
            disp(['CTL P1 Vg=', num2str(round(10*Vgctl1)/10), ' Ve, Zg=', num2str(Zgctl), ' Ohm, IL=',
num2str(IL*1e3), ' mAe, Vg=', num2str(round(10*Vgctl2)/10), ' Ve ']);
        end
    case {5,6}
        ZL=(40-X)*(1+1i);
        Zg=(20+X)*(1-1i);
        VL=Vg*ZL/(ZL+Zg);
        ILmod=abs(VL/ZL);
        ILphase=angle(VL/ZL)*180/pi;
        disp(['DATOS Vg=', num2str(round(10*Vg)/10), ' Ve, ZL=', num2str(ZL), ' Ohm.
Zg=', num2str(Zg), ' Ohm']);
        disp(['SOL P1 VL=', num2str(round(10*VL)/10), ' Ve. ILmod=', num2str(round(10*ILmod*1e3)/10),
mAe, Fase IL=', num2str(round(10*ILphase)/10), ' grados']);
        %control
        if flag_control==1
            ILctl=ILmod*exp(1i*ILphase*pi/180);
```

```

        ZLct1=VL/ILct1;
        Zgct1=(Vg-VL)/ILct1;
        Vgct1=VL+ILct1*Zgct1;
        disp(['CTL P1 Vg=', num2str(round(10*Vgct1)/10), ' Ve, ZL=', num2str(ZLct1), ' Ohm, ZgL=',
num2str(Zgct1), ' Ohm']);
        end

    case {7,8}
        Zg=(40-X)*(1+1i);
        VL=5-3*1i;
        IL=(Vg-VL)/Zg; %Ig=IL
        ZL=Zg*VL/(Vg-VL);
        disp(['DATOS Vg=', num2str(round(10*Vg)/10), ' ve, Zg=', num2str(Zg), ' Ohm. VL=', num2str(VL), '
Ve']);
        disp(['SOL P1 IL=', num2str(round(10*IL*1e3)/10), ' mAe. ZL=', num2str(round(10*ZL)/10), ' Ohm']);
        %control
        if flag_control==1
            Zgct1=(Vg-VL)/IL;
            VLct11=Vg-IL*Zg; VLct12=IL*ZL;
            Vgct1=VLct11+IL*Zg;
            disp(['CTL P1 Vg=', num2str(round(10*Vgct1)/10), ' Ve, Zg=', num2str(Zgct1), ' Ohm, VL=',
num2str(VLct11), ' Ve, VL=', num2str(VLct12), ' Ve ']);
            end

    case {9,0}
        ZL=(30-X)*(1-1i);
        Zg=(20+X)*(1+1i);
        IL=Vg/(ZL+Zg);
        VLmod=abs(IL*ZL);
        VLphase=angle(IL*ZL)*180/pi;
        disp(['DATOS Vg=', num2str(round(10*Vg)/10), ' Ve, ZL=', num2str(ZL), ' Ohm.
Zg=', num2str(Zg), ' Ohm']);
        disp(['SOL P1 IL=', num2str(round(10*IL*1e3)/10), ' mAe. VLmod=', num2str(round(10*VLmod)/10), '
Ve, Fase VL=', num2str(round(10*VLphase)/10), ' grados']);
        %control
        if flag_control==1
            VLct1=VLmod*exp(1i*VLphase*pi/180);
            ZLct1=VLct1/IL;
            Zgct1=(Vg-VLct1)/IL;
            Vgct1=VLct1+IL*Zgct1;
            disp(['CTL P1 Vg=', num2str(round(10*Vgct1)/10), ' Ve, ZL=', num2str(ZLct1), ' Ohm, ZgL=',
num2str(Zgct1), ' Ohm']);
            end
    end

disp(' ')
disp('PROBLEMA 2')
switch switch_cases
    case {1,2}
        ZL=(30+Y)*(1+1i); VL=20*(1-1i);
        YL=1/ZL; IL=VL/ZL;
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['DATOS P2: ZL=', num2str(ZL), ' Ohm, VL=', num2str(VL), ' Ve'])
        disp(['SOL P2 PL=', num2str(round(10*PL)/10), ' W']);
    case {3,4}
        YL=(40+Y)*(2-1i)*1e-3; IL=700*(1+2i)*1e-3;
        ZL=1/YL; VL=IL*ZL;
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['DATOS P2: YL=', num2str(YL*1e3), ' mS, IL=', num2str(IL*1e3), ' mAe'])
        disp(['SOL P2 PL=', num2str(round(10*PL)/10), ' W']);
    case {5,6}
        VL=(30-Y)*(2+1i); IL=(400+10*Y)*(3-1i)*1e-3;
        ZL=VL/IL; YL=IL/VL;
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['DATOS P2: VL=', num2str(VL), ' Ve, IL=', num2str(IL*1e3), ' mAe'])
        disp(['SOL P2 PL=', num2str(round(10*PL)/10), ' W']);
end

```

```

case {7,8}
YL=(30+Y)*(1+1i)*1e-3; IL=200*(2+i)*1e-3;
ZL=1/YL; VL=IL*ZL;
PL=real(VL*conj(IL));
PLct11=abs(VL)^2*real(YL);
PLct12=abs(IL)^2*real(ZL);
if PL-PLct11>1e-12 || PL-PLct12>1e-12
    disp('ERROR')
end
disp(['DATOS P2: YL=', num2str(YL*1e3),' mS, IL=', num2str(IL*1e3),' mAe'])
disp(['SOL P2 PL=', num2str(round(10*PL)/10), ' W']);
case {9,0}
ZL=(40-Y)*(2+1i); VL=30*(2-1i);
YL=1/ZL; IL=VL/ZL;
PL=real(VL*conj(IL));
PLct11=abs(VL)^2*real(YL);
PLct12=abs(IL)^2*real(ZL);
if PL-PLct11>1e-12 || PL-PLct12>1e-12
    disp('ERROR')
end
disp(['DATOS P2: ZL=', num2str(ZL),' Ohm, VL=', num2str(VL),' Ve'])
disp(['SOL P2 PL=', num2str(round(10*PL)/10), ' W']);
end

disp(' ')
disp('PROBLEMA 3')
%Datos comunes
Vg=10+Y;
Rg=50; R=100; C=20/pi*1e-12; L=100/pi*1e-9;
f=(500+10*X)*1e6;
ZC=-1i/(2*pi*f*C); YC=1/ZC;
ZB=1i*2*pi*f*L; YB=1/ZB;
disp(['DATOS P3: f=', num2str(f/1e6),' MHz, Vg=', num2str(Vg),' Ve']);
switch switch_cases
    case {1,2}
        ZL=R+ZB; YL=1/ZL;
        IL=Vg/(Rg+ZL);
        VL=Vg*ZL/(ZL+Rg);
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['SOL P2 YL=', num2str(round(10*YL*1e3)/10),' mS, PL=', num2str(round(10*PL*1e3)/10), '
mW']);
    case {3,4}
        YL=1/R+YB; ZL=1/YL;
        IL=Vg/(Rg+ZL);
        VL=Vg*ZL/(ZL+Rg);
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['SOL P2 ZL=', num2str(round(10*ZL)/10),' Ohm, PL=', num2str(round(10*PL*1e3)/10), ' mW']);
    case {5,6}
        YL=1/R+YC; ZL=1/YL;
        IL=Vg/(Rg+ZL);
        VL=Vg*ZL/(ZL+Rg);
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['SOL P2 ZL=', num2str(round(10*ZL)/10),' Ohm, PL=', num2str(round(10*PL*1e3)/10), ' mW']);
    case {7,8}
        ZL=R+ZC; YL=1/ZL;
        IL=Vg/(Rg+ZL);
        VL=Vg*ZL/(ZL+Rg);
        PL=real(VL*conj(IL));
        PLct11=abs(VL)^2*real(YL);
        PLct12=abs(IL)^2*real(ZL);
        if PL-PLct11>1e-12 || PL-PLct12>1e-12
            disp('ERROR')
        end
        disp(['SOL P2 YL=', num2str(round(10*YL*1e3)/10),' mS, PL=', num2str(round(10*PL*1e3)/10), '
mW']);
end

```

```

case {9,0}
    ZL=R+ZB; YL=1/ZL;
    IL=Vg/(Rg+ZL);
    VL=Vg*ZL/(ZL+Rg);
    PL=real(VL*conj(IL));
    PLct11=abs(VL)^2*real(YL);
    PLct12=abs(IL)^2*real(ZL);
    if PL-PLct11>1e-12 || PL-PLct12>1e-12
        disp('ERROR')
    end
    disp(['SOL P2 YL=', num2str(round(10*YL*1e3)/10), ' mS, PL=', num2str(round(10*PL*1e3)/10), '
mW']);

end
disp(' ')
disp('PROBLEMA 4')
%Datos comunes
Vg=10/sqrt(2); %Eficaz
Rg=50;

switch switch_cases
    case {1,2}
        t1=0.926e-9; I1=89.44e-3;
        t3=1.426e-9; I3=-89.44e-3;
        T=2*(t3-t1); f=1/T;
        phi_I=2*pi-2*pi*f*t1;
        na=floor(phi_I/2/pi);
        phi_I=phi_I-na*2*pi;
        I=I1/sqrt(2)*exp(1i*phi_I); %Fasor de amplitud eficaz
        VL=Vg-I*Rg;
        Vp=abs(VL); %eficaz
        disp(['SOL P3 f=', num2str(round(f/1e6)), ' MHz, phi_I=', num2str(round(10*phi_I*180/pi)/10), '°,
Vp=', num2str(round(10*Vp*sqrt(2))/10), ' V pico']);

    case {3,4}
        t4=1.676e-9; I4=0;
        t5=1.926e-9; I5=89.44e-3;
        T=4*(t5-t4); f=1/T;
        Ip=I5/sqrt(2);
        phi_I=2*pi-2*pi*f*t5;
        %na=floor(phi_I/2/pi);
        %phi_I=phi_I-na*2*pi;
        I=Ip*exp(1i*phi_I); %Fasor de amplitud eficaz
        VL=Vg-I*Rg;
        %Vp=abs(VL); %eficaz
        phi_V=angle(VL);
        na=floor(phi_V/2/pi);
        phi_V=phi_V-na*2*pi;
        disp(['SOL P3 f=', num2str(round(f/1e6)), ' MHz, Ip=', num2str(round(10*Ip*1e3)/10), ' mA
eficaces, phi_V=', num2str(round(100*phi_V)/100), ' rad'  ]);
    case {5,6}
        t2=1.176e-9; I2=0;
        t3=1.426e-9; I3=-89.44e-3;
        T=4*(t3-t2); f=1/T;
        phi_I=pi/2-2*pi*f*t2;
        na=floor(phi_I/2/pi);
        phi_I=phi_I-na*2*pi;
        I=-I3/sqrt(2)*exp(1i*phi_I); %Fasor de amplitud eficaz
        VL=Vg-I*Rg;
        Vp=abs(VL); %eficaz
        disp(['SOL P3 f=', num2str(round(f/1e6)), ' MHz, phi_I=', num2str(round(100*phi_I)/100), 'rad,
Vp=', num2str(round(10*Vp)/10), ' V eficaces']);

    case {7,8}
        t3=1.426e-9; I3=-89.44e-3;
        t6=2.426e-9; I6=-89.44e-3;
        T=(t6-t3); f=1/T;
        phi_I=pi-2*pi*f*t3;
        na=floor(phi_I/2/pi);
        phi_I=phi_I-na*2*pi;
        I=-I3/sqrt(2)*exp(1i*phi_I); %Fasor de amplitud eficaz
        VL=Vg-I*Rg;
        Vp=abs(VL); %eficaz
        disp(['SOL P3 f=', num2str(round(f/1e6)), ' MHz, phi_I=', num2str(round(10*phi_I*180/pi)/10), '°,
Vp=', num2str(round(10*Vp*sqrt(2))/10), ' V pico']);

    case {9,0}
        t5=1.926e-9; I5=89.44e-3;
        t6=2.426e-9; I6=-89.44e-3;
        T=2*(t6-t5); f=1/T;
        phi_I=2*pi-2*pi*f*t5;

```

```

    %na=floor(phi_I/2/pi);
    %phi_I=phi_I-na*2*pi;
    I=I5/sqrt(2)*exp(1i*phi_I); %Fasor de amplitud eficaz
    Ip=I5/sqrt(2);
    VL=Vg-I*Rg;
    Vp=abs(VL); %eficaz
    phi_V=angle(VL);
    na=floor(phi_V/2/pi);
    phi_V=phi_V-na*2*pi;
    disp(['SOL P3 f=', num2str(round(f/1e6)), ' MHz, Ip=', num2str(round(10*Ip*1e3*sqrt(2))/10), ' mA
pico, phi_V=', num2str(round(10*phi_V*180/pi)/10), ' °  ']);

end
disp(' ')
%Problema opcional:
YL=I/VL;
RL=1/real(YL);
BL=imag(YL); CL=BL/2/pi/f;
disp(['SOL Opcional RL=', num2str(round(RL*10)/10), ' Ohm, CL=', num2str(round(CL*1e12*pi)), '/pi
pF']);
disp(' ')
flag_loop_ON=1;
end
return

```